

# DIGITAL DESIGN WITH HDL

## Chapter 5: Behavioral model



# Behavioral model

- Use procedural blocks: **initial**, **always**
- These blocks contain series of statements
  - Abstract – works \*somewhat\* like software
  - Be careful to still remember it's hardware!
- Parallel operation **across** blocks
  - All blocks in a module operate simultaneously
- **Sequential** or **parallel** operation **within blocks**
  - Depends on the way the block is written
  - Discuss this in a later lecture
- **LHS of assignments are variables** (**reg**)



# Procedural blocks

- **initial**
  - Behavioral block operates **ONCE**
  - Starts at time 0 (beginning of operation)
  - Useful for test benches
  - Can sometimes provide **initialization of memories/FFs**
    - Often better to use “reset” signal
  - Inappropriate for combinational logic
  - Usually **cannot be synthesized**
- **always**
  - Behavioral block operates **CONTINUOUSLY**
  - Can use a **trigger list** to control operation; `@(a, b, c)`
  
# initial vs. always

```
reg [3:0] v1, v2, v3, v4;  
initial begin  
    v1 = 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
    #2 v4 = v3 + 1;  
    v1 = v4 + 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
end
```

```
reg [3:0] v1, v2, v3, v4;  
always begin  
    v1 = 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
    #2 v4 = v3 + 1;  
    v1 = v4 + 1;  
    #2 v2 = v1 + 1;  
    v3 = v2 + 1;  
end
```



# always blocks

- General syntax:

```
always [<trigger list>] begin  
    <Procedural statements>  
end
```

- Operates **continuously** or on a **trigger list** (sensitive list/event control list)
- Can be used with **initial** blocks or other **always** blocks
  - Unlimited in a module
  - All are executed in parallel
- Cannot “nest” **initial** or **always** blocks

# Trigger lists

- Continuously check the trigger list in an **always** block to trigger the block
- Start with an event control operator: @
- Contain **signals**, **not expressions**
  - Scalar or vector
  - Net or register
- Type of trigger lists
  - **Level trigger**: combinational circuits/blocks
  - **Edge trigger**: sequential circuits/blocks
  - One module can include both

# Level trigger

- Syntax:
  - Old style:  $\text{@}(\text{<signal 1> or <signal 2> or ... or <signal n>})$
  - New style:  $\text{@}(\text{<signal 1>, <signal 2>, ..., <signal n>})$
- Operations:
  - When **any signal changes**, statements in the block are executed
  - Otherwise, keep the values of LHS unchanged
- **Special case:**  $\text{@}(\text{*})$ 
  - When all signals in RHS and conditional statements are in the trigger list

# Examples

```
always @(x1 or x2 or x3)
  z1 = #5 (x1 & x2 & x3);
```

```
always @(in1, in0, sel) begin
  if (sel == 1'b0) out = in0;
  else out = in1;
end
```

```
always @ (a or b or cin) begin
  sum = a + b + cin;
  cout = (a[3] & b[3]) |
    ((a[3] | b[3]) & (a[2] & b[2])) |
    ((a[3] | b[3]) & (a[2] | b[2]) & (a[1] & b[1])) |
    ((a[3] | b[3]) & (a[2] | b[2]) & (a[1] | b[1])
      & (a[0] & b[0])) |
    ((a[3] | b[3]) & (a[2] | b[2]) & (a[1] | b[1])
      & (a[0] | b[0]) & cin);
end
```

```
always @(a, b, c) begin
  a1 = a & b;
  a2 = b & c;
  a3 = a & c;
  carry = a1 | a2 | a3;
end
```



# Example

- Design and implement an adder-4bit



```
module adder4b (Sum, Cout, A, B, Cin);  
  input  [3:0] A, B;  
  input  Cin;  
  output reg [3:0] Sum;  
  output reg Cout;  
  always @(A, B, Cin)  
    {Cout, Sum} = A + B + Cin;  
endmodule
```

# Edge trigger

- Used to detect edges of signals
  - Rising edge: **posedge**
    - $0, x, z \rightarrow 1$
  - Falling edge: **negedge**
    - $1, x, z \rightarrow 0$
- Syntax:
  - Old style: **@(posedge/negedge <signal 1> or posedge/negedge <signal 2> or ... or posedge/negedge <signal n>)**
  - New style: **@(posedge/negedge <signal 1>, posedge/negedge <signal 2>, ..., posedge/negedge <signal n>)**
- Operations:
  - When **any signal in the list changes accordingly to the edge detect operator**, statements in the block are executed
  - Otherwise, all LHS variables are kept unchanged

# Examples

```
always @(posedge clk)
  q <= d;
```


```
always @(posedge clk or negedge rst_n) begin
  if (rst_n == 0)
    count <= 4'b0000;
  else
    count <= (count + 1) % 16;
end
```

```
always @(posedge clk, posedge rst_n) begin
  if (rst_n == 1)
    y <= 4'b0000;
  else
    y <= d;
end
```

```
always @(posedge clk) begin
  if (rst_n == 0)
    q <= 1'b0;
  else
    q <= d;
end
```
 
# Example

- Design and implement a simple D flip flop




```
module dff(D, clk, Q, Qbar);  
  input D, clk;  
  output reg Q, Qbar;  
  always @(posedge clk) begin  
    Q <= D;  
    Qbar <= ~D;  
  end
```

# Control vs. Clock signals


- Clock signal: **synchronize** behaviors of a module
  - **Always included** in trigger lists
  - No need to check inside the block
  - Rising or falling edges
- Control signal: **handle** operations of a module
  - E.g., reset/clear or set/preset signals
  - **Sometimes included** in trigger lists; **sometimes not**
  - Always checked inside the block
  - Active low or active high
 
# Control signals

- **Synchronous** control signals
  - Need to **wait for clock edges** to handle the module



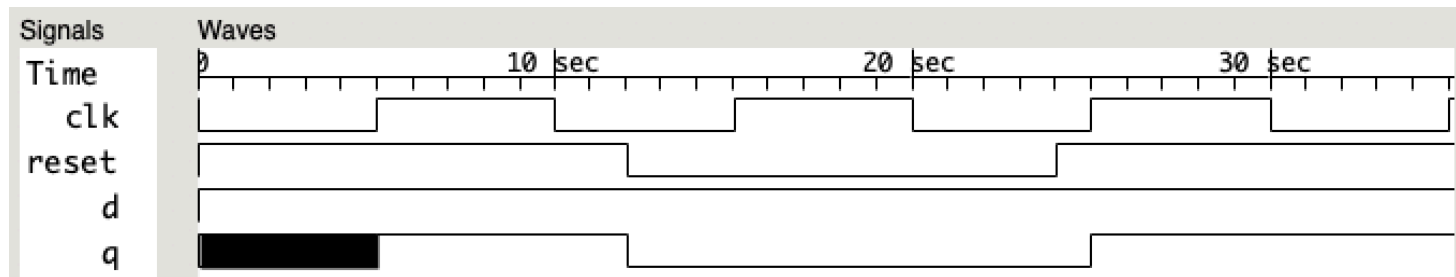- **Asynchronous** control signals
  - Handle the module **right after active**



# Control signals in Verilog

- **Synchronous** control signals
  - **Do not include** in trigger lists
  - Active time should be at least **1 cycle**
- **Asynchronous** control signals
  - **Must include** in trigger lists, need **posedge/negedge**
    - Active low: **negedge**
    - Active high: **posedge**
  - Active time can be arbitrary

```
always @(posedge clk)
    if (reset == 0) q <= 0;
    else q <= d;
```

```
always @(posedge clk, negedge reset)
    if (reset == 0) q <= 0;
    else q <= d;
```

What happen when there is no “negedge”  
is associated with the reset signal?

# Procedural assignments

- A statement that **assigns values to register variables** is called a procedural assignment
  - LHS: register, bit-select, part-select, or concatenation
    - To assign to output: **output reg [3:0] a;**
  - Take place within an **initial** block or an **always** block
  - RHS is evaluated and **scheduled to be assigned** to LHS at a time specified by an optional timing control

Procedural Assignment	Continuous Assignment
Occurs within an <b>initial</b> or an <b>always</b> statement	Not used in an <b>initial</b> or an <b>always</b> statement
Operates with respect to other statements in the <b>initial</b> or <b>always</b> block	Executes concurrently with other statements
Drives registers	Drives nets
Uses blocking (=) or nonblocking (<=) symbols	Uses the assignment (=) symbol




# Blocking assignments

- A **blocking assignment** needs to complete execution before the next statement executes
  - “=” is used for blocking assignment
  - Assignments are performed **sequentially**
    - Order of assignment is very important
  - Used with **level-trigger always** blocks to describe **combinational circuits**
  - Used in **initial** blocks
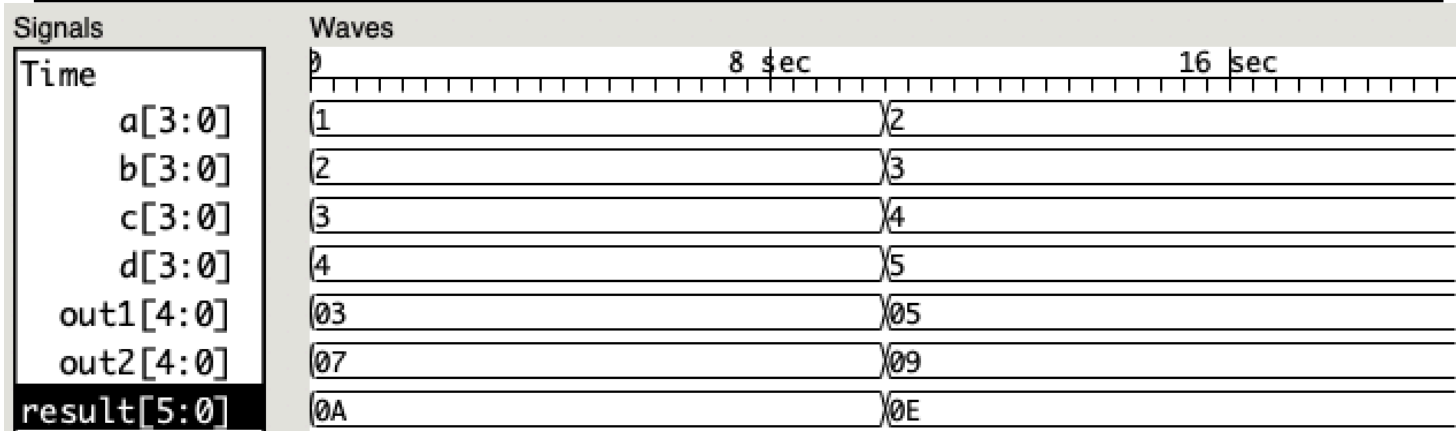
# Example

```
module add_seq(input [3:0] a, b, c, d, output reg [5:0] result);  
  reg [4:0] out1, out2;  
  always @(a, b, c, d) begin  
    out1 = a + b;  
    out2 = c + d;  
    result = out1 + out2;  
  end  
endmodule
```




# Non-blocking assignments

- **Non-blocking assignments** allow multiple assignments to be performed **without blocking** each others
  - “<=” is used for non-blocking assignments
  - Assignments are performed in **parallel**
    - Order of assignments is NOT important
  - Used with **edge trigger** **always** blocks to describe **sequential circuits**
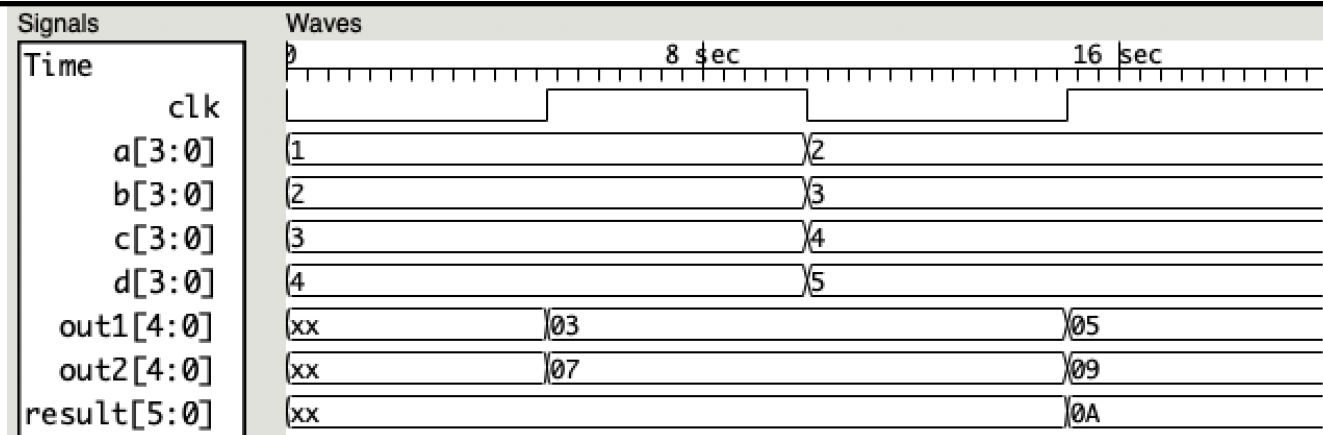
# Example

```
module add_par(input clk, input [3:0] a, b, c, d, output reg [5:0] result);  
  reg [4:0] out1, out2;  
  always @(posedge clk) begin  
    out1 <= a + b;  
    out2 <= c + d;  
    result <= out1 + out2;  
  end  
endmodule
```



# Blocking vs. Non-blocking example

- Assume initially that A=1, B=2, C=3, and D=4

```
reg [7:0] A, B, C, D;  
always @(posedge clk)  
begin  
    A = B + C;  
    B = A + D;  
    C = A + B;  
    D = B + D;  
end
```

Correct in results but **don't use blocking in edge trigger**

```
reg [7:0] A, B, C, D;  
always @(posedge clk)  
begin  
    A <= B + C;  
    B <= A + D;  
    C <= A + B;  
    D <= B + D;  
end
```

**Incorrect in results** but **use non-blocking in edge trigger**

# Correcting the example

```
reg [7:0] A, B, C, D;  
reg [7:0] newA, newB, newC, newD;  
always @(posedge clk)  
begin  
    A <= newA; B <= newB;  
    C <= newC; D <= newD;  
end  
always @(*) begin  
    newA = B + C;  
    newB = newA + D;  
    newC = newA + newB;  
    newD = newB + D;  
end
```

```
reg [7:0] A, B, C, D;  
always @(posedge clk)  
begin  
    A <= B + C;  
    B <= B + C + D;  
    C <= B + C + B + C + D;  
    D <= B + C + D + D;  
end
```

# Why non-blocking in sequential?

```
always @ (posedge clk, posedge rst) // behavior1
    if (rst) y1 = 0; //reset
    else    y1 = y2;
always @ (posedge clk or posedge rst) // behavior2
    if (rst) y2 = 1; // preset
    else    y2 = y1;
```

- If behavior1 always first after reset,  $y1 = y2 = 1$
- If behavior2 always first after reset,  $y2 = y1 = 0$ .
- Results are order dependent, **ambiguous – race condition!**
- This is why we don't use blocking assigns for flip-flops...

# Correcting the example

```
always @ (posedge clk, posedge rst) // behavior1
  if (rst) y1 <= 0; //reset
  else    y1 <= y2;
always @ (posedge clk or posedge rst) // behavior2
  if (rst) y2 <= 1; // preset
  else    y2 <= y1;
```

- Assignments for y1 and y2 occur in **parallel**
- y1 = 1 and y2 = 0 after reset
- Values swap each clock cycle after the reset
- **No race condition!**



# Control statements

- Behavioral Verilog looks a lot like software
  - risk! – danger and opportunity
- Provides similar control structures
  - Not all of these actually synthesized, but some non-synthesizable statements are useful in test benches
- What kinds synthesize?
  - if
  - case
  - for loops with constant bounds
- **Must be placed inside a procedural block**

# if - else if - else

- Operator ? : for simple conditional assignments
- Sometimes need more complex behavior, can use if statement!
  - Does not conditionally “execute” block of “code”
  - Does not conditionally create hardware!
  - It makes a multiplexer or similar logic
- Generally:
  - Hardware for all paths is created
  - All paths produce their results in parallel
  - One path’s result is selected depending on the condition

# if - else if - else

- Syntax: `if (expression) statement1;`

```
if (x1 & x2) z1 = 1;
```

```
if (expression) statement1;  
else statement2;
```

```
if (rst_n == 0)  
    ctr = 3'b000;  
else ctr = next_count;
```

```
if (expression1) statement1;  
else if (expression2) statement2;  
else if (expression3) statement3;  
else default statement;
```


```
if (opcode == 2'b 00)  
    z1 = x1 + x2 ;  
else if (opcode == 2'b01)  
    z1 = x1 - x2 ;  
else if (opcode == 2'b10)  
    z1 = x1 * x2 ;  
else  
    z1 = x1 / x2 ;
```

# Issues with if - else if - else

- Priority check
- Chain of multiplexers can be used: **degrade performance**

```

 
if (x == 4'b0001) y = 2'b00;
else if (x == 4'b0010) y = 2'b01;
else if (x == 4'b0100) y = 2'b10;
else if (x == 4'b1000) y = 2'b11;
else y = 2'bxx;
    
```



- **Un-wanted latch** when failing to fully specify all possible cases (combinational circuits)

```

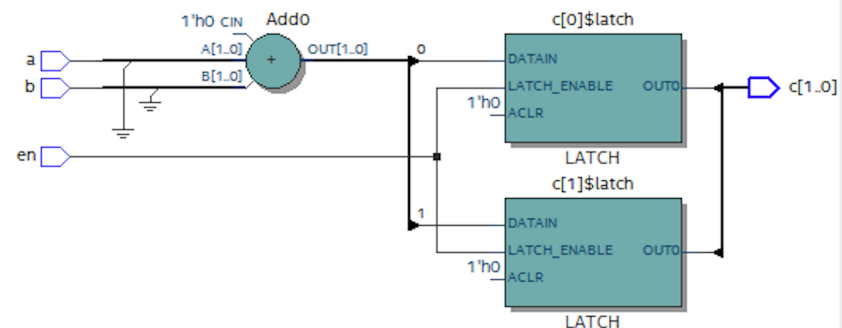always @(en, a, b) begin
  if (en) c = a + b;
end
    
```



# Case statements

- Verilog has three types of case statements:
  - `case`, `caseX`, and `caseZ`
- Performs bitwise match of expression and case item
  - Both must have **same bitwidth** to match!
- Syntax:

```
case (expression)
    case_item1 : procedural_statement1;
    case_item2 : procedural_statement2;
    case_item3 : procedural_statement3;
    ...
    case_itemn : procedural_statementn;
    default : default_statement;
endcase
```

# Case statements

- **casex**
  - The values of x or z are treated as “don’t care”
- **casez**
  - The value of z is treated as “don’t care”
  - The value of x is a special value


```
reg [7:0] r, mask;  
mask = 8'b0x0x0x0x0;  
casex (r ^ mask)  
    8'b001100xx: stat1;  
    8'b1100xx00: stat2;  
    8'b00xx0011: stat3;  
    8'bx010100: stat4;  
endcase
```

```
reg [7:0] ir;  
casez (ir)  
    8'b1??????? : instruction1(ir);  
    8'b01??????? : instruction2(ir);  
    8'b00010???? : instruction3(ir);  
    8'b000001??? : instruction4(ir);  
endcase
```
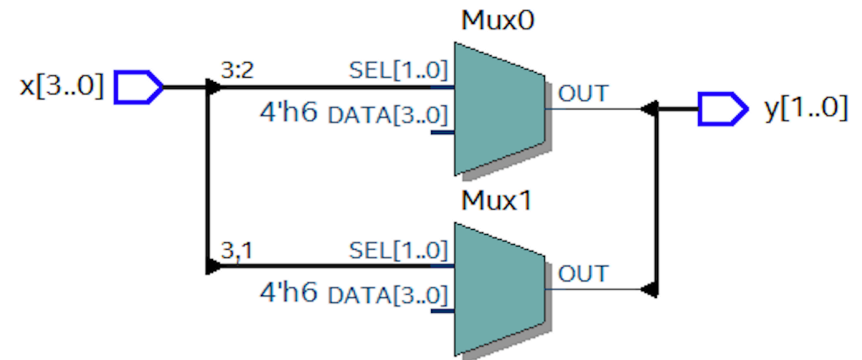
# Case statements

- Can help in **reducing chain of multiplexers**

```
case (x)
  4'b0001: y = 2'b00;
  4'b0010: y = 2'b01;
  4'b0100: y = 2'b10;
  4'b1000: y = 2'b11;
  default: y = 2'bxx;
endcase
```



- Reduce code lines compared to if
- May introduce **un-wanted latch** (like **if**)

```
module priority_encoder (output reg [1:0] Code,
                        input [3:0] Data);
  always @(Data)
    casex (Data)
      4'b1xxx : Code = 3;
      4'b01xx : Code = 2;
      4'b001x : Code = 1;
      4'b0001 : Code = 0;
      default : Code = 3'bxxx;
    endcase
endmodule
```