

DIGITAL DESIGN WITH HDL

Chapter 4: RTL model



RTL Verilog

- Higher-level of description than the structural model
 - Don't always need to specify each individual gate
 - Can take advantage of **operators**
 - **Used to design combinational logic only**
- More hardware-explicit than the behavioral model
 - Doesn't look as much like software
 - Frequently easier to understand what's happening
- Very **easy to synthesize**
 - Supported by even primitive synthesizers
 - **Note:** not all operators can be synthesized

Continuous assignments

- Syntax:

```
assign [#delay] lhs_net = rhs_expression;
```

- Occur **outside** procedural blocks (**initial** or **always**)
- Operation:
 - Whenever the value of a variable in **rhs** changes, **rhs** is evaluated and assigned to **lhs** after the **delay** interval
- Example:

```
wire out, a, b;  
assign out = a & b;
```

- Continuous: **rhs** is constantly operating

The lhs_net

- The left-hand-side can be:
 - Scalar nets
 - Vector nets
 - Single bits of vector nets
 - Part-selects of vector nets
 - Concatenation of any of the above
- Examples:

```
wire [7:0] out, val;  
wire [7:0] a, b;  
assign out[7:4] = a[3:0] | b[7:4]; //vector nets  
assign val[3] = c & d; //single bits of vector nets  
assign {a, b} = stimulus[15:0]; //concatenation of scalar nets
```

- Cannot be used to assign a value to a register

The rhs_expression

- Variables/signals in the right-hand-side can be
 - Registers: scalars and vectors
 - Nets: scalars and vectors
 - Function calls

- Example

```
wire x1, x2, x3, x;  
assign x = (x1&x2)|x3;
```

```
reg [3:0] a, b  
wire [3:0] sum;  
assign sum = a + b;
```


- Can also be a pass-through/alias

```
assign a = stimulus[16:9];
```

- **note:** “aliasing” is only one direction

 
Example

- Design and test a module of the following circuit



```
module log_eqn_sop (x1, x2, x3, x4, z1);  
    input x1, x2, x3, x4;  
    output z1;  
  
    assign z1 = (x1&~x2) | (~x3&x4) | (x2&x3);  
endmodule
```
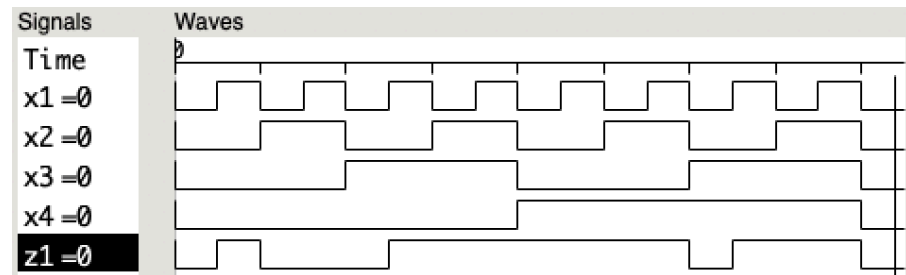
```
module log_eqn_sop_tb;  
    reg [5:1] x; //combine stimulus  
    wire z1;  
    initial for (x = 0; x < 16; x = x + 1) #5;  
        log_eqn_sop inst1(.x1(x[1]),.x2(x[2]),  
                        .x3(x[3]),.x4(x[4]),.z1(z1));  
endmodule
```



Expression in Verilog

- Expressions consist of **operands** and **operators**
 - The value of an expression is determined from the combined operations on the operands
 - The value of an expression can be assigned to a left-hand-side net or register variable
 - Continuous assignments: net
 - **assign**
 - Procedural assignments: register
 - In **initial** or **always** blocks

Operands

Operands	Comments	Example
Constant	Signed or unsigned	4'b1010; -10
Parameter	Similar to a constant	parameter a = 4'b1010
Net	Scalar or vector	wire a; wire [3:0] b;
Register	Scalar or vector	reg a; reg [3:0] b;
Bit-select	One bit from a vector	a[0]; a[1]
Part-select	Contiguous bits of a vector	a[3:1]; a[2:0]
Memory element	One word of a memory	mem[0];
Function call	System or user function	func(a,b);

Constant


- Constant can be signed or unsigned
 - A **decimal integer**: a signed number
 - An integer **specified by a base**: an unsigned number

Constant	Comments
127	Signed decimal: Value = 8-bit binary vector: 8'b0111_1111
-1	Signed decimal: Value = 8-bit binary vector: 8'b1111_1111
-128	Signed decimal: Value = 8-bit binary vector: 8'b1000_0000
4'b1110	Binary base: Value = unsigned decimal 14
8'b0011_1010	Binary base: Value = unsigned decimal 58
16'h1A3C	Hexadecimal base: Value = unsigned decimal 6716
16'hBCDE	One word of a memory
9'O536	Octal base: Value = unsigned decimal 350
-22	Signed decimal: Value = 8-bit binary vector: 8'b1110_1010
- 9'o352	Octal base: Value = 8-bit binary vector: 1110_1010 = unsigned decimal 234

Memory element

- A memory element refers to a **word** in memory
 - One or more bits
 - **Referenced by words only** - no bit-/part-select
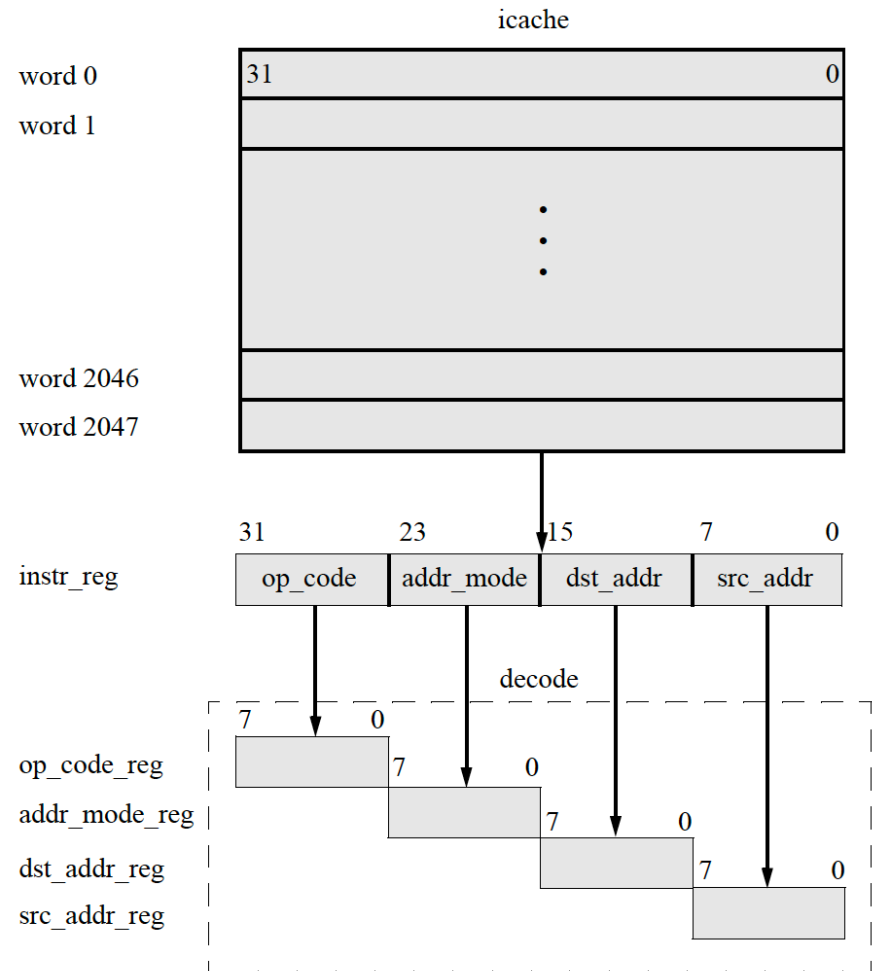
```
reg [31:0] icache [0:2047]; //memory
reg [31:0] instr_reg;
instr_reg = icache [127];
op_code_reg = instr_reg [31:24];
```



Operators

Type	Symbol	Operation	# operands	Example
Arithmetic	+	Add	2 or 1	$a + b$; +5
	-	Subtract	2 or 1	$a - b$; -10
	*	Multiply	2	$a * b$;
	/	Divide	2	a / b ;
	%	Modulus	2	$a \% b$;
Logical	&&	Logical and	2	$a \&\& b$;
		Logical or	2	$a b$;
	!	Logical negation	1	!a;
Relational	>	Greater than	2	$a > b$;
	<	Less than	2	$a < b$;
	>=	Greater than or equal	2	$a >= b$;
	<=	Less than or equal	2	$a <= b$;

Operators (cont.)

Type	Symbol	Operation	# operands	Example
Equality	==	Logical equality	2	a == b;
	!=	Logical inequality	2	a != b;
	===	Case equality	2	a === b;
	!==	Case inequality	2	a !== b;
Bitwise	&	Bitwise and	2	a & b;
		Bitwise or	2	a b;
	~	Bitwise negation	1	~a
	^	Bitwise Exclusive-or	2	a ^ b;
	~^ or ~^	Bitwise Exclusive-nor	2	a ~^ b; a ~^ b;
Reduction	&	AND	1	&a;
	^&	NAND	1	^&a;
		OR	1	a;
	^	NOR	1	^ a;
	^	Exclusive-OR	1	^a
	^~ or ~^	Exclusive-NOR	1	~^a; ^~a;

Operators (cont.)

Type	Symbol	Operation	# operands	Example
Shift	<<	Shift left	2	<code>a << 5;</code>
	>>	Shift right	2	<code>a >> 4;</code>
Conditional	?:	Conditional	2	<code>a ? b + c : d + e;</code>
Concatenation	{}	Concatenation	2 or more	<code>{a,b,c}</code>
Replication	{ {} }	Replication	2 or more	<code>{3{a}}</code>

Arithmetic operators

- Perform on one (unary) or two (binary) operands
 - Radices: binary, octal, decimal, or hexadecimal
 - Integer or real operands: **signed** (2's complement)
 - Integer register: **signed**
 - Register and net operands: **unsigned**
- Size of results
 - Multiply operator: `sizeof(op1) + sizeof(op2)`
 - Others: `sizeof(the largest operand)`

Addition		Subtraction		Multiplication		Division	
Augend		Minuend		Multiplicand		Dividend	
+) Addend		–) Subtrahend		×) Multiplier		÷) Divisor	
Sum		Difference		Product		Quotient, Remainder	

Example

```

module arith(a, b, op, result);
  input [3:0] a, b;
  input [2:0] op;
  output reg [7:0] result;
  always @ (a or b or op) begin
    case (op)
      3'b000: result = a + b;
      3'b001: result = a - b;
      3'b010: result = a * b;
      3'b011: result = a / b;
      3'b100: result = a % b;
    endcase
  end
endmodule

```

a = 0011, b = 1111, opcode = 000, rslt = 00010010
 a = 1111, b = 1111, opcode = 001, rslt = 00000000
 a = 1110, b = 1110, opcode = 010, rslt = 11000100
 a = 1000, b = 0010, opcode = 011, rslt = 00000100
 a = 0111, b = 0011, opcode = 100, rslt = 00000001

Signals		Waves				
Time		0 10 sec 20 sec				
a[3:0]	=	0011	1111	1110	1000	0111
b[3:0]	=	1111	1110	0010	0011	
opcode[2:0]	=	000	001	010	011	100
rslt[7:0]	=	00010010	00000000	11000100	00000100	00000001

Logical vs. Bitwise


- Consider **operands as logical values** (true/false)
 - Nonzero operands: **true** (without any **x** or **z** bit)
 - Zero operands or ambiguous bit (**x/z**): **false**
- Results are always **1** bit
 - True: **1**
 - False: **0**
- Consider **operands as vector/scalar** values
 - Apply operators bit by bit
- Size of results = size of the largest operand
 - Insert **0** bits to smaller operands
- Results store: **0, 1, or x**

Example

```

module bitwise;
  reg [3:0] a, b;
  wire [3:0] rslt_bw_and, rslt_bw_or, rslt_bw_not, rslt_bw_xor, rslt_bw_xnor;
  wire rslt_log_and, rslt_log_or, rslt_log_not;
  assign rslt_bw_and = a&b;
  assign rslt_bw_or = a|b;
  assign rslt_bw_not = ~a;
  assign rslt_bw_xor = a^b;
  assign rslt_bw_xnor = a~^b;
  assign rslt_log_and = a&&b;
  assign rslt_log_or = a||b;
  assign rslt_log_not = !a;
endmodule

```

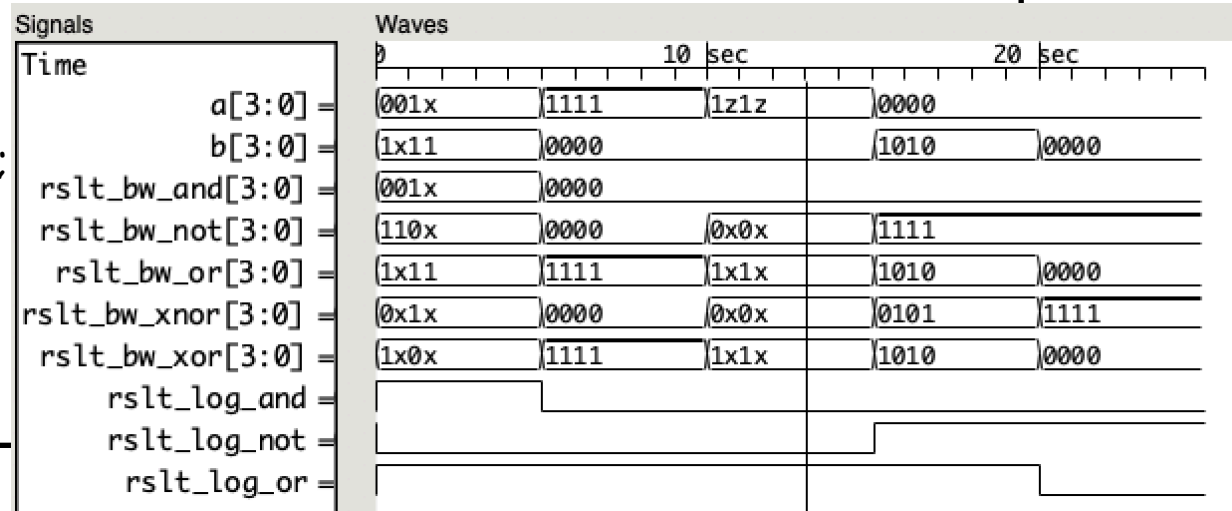


Relational

- Compare and return a logical value:
 - 1: true
 - 0: false
- Rules of operands
 - Net or register operands are **unsigned**
 - Real or integer operands are **signed** values
 - Any **x** or **z** bit in an operand return a result of **x**
 - Zero-extended for the smaller operand

 Example

```
module comparator_assign(a, b, a_lt_b, a_lte_b, a_gt_b, a_gte_b);  
    input [3:0] a, b;  
    output      a_lt_b, a_gt_b, a_lte_b, a_gte_b;  
  
    assign a_lt_b = a < b;  
    assign a_lte_b = a <= b;  
    assign a_gt_b = a > b;  
    assign a_gte_b = a >= b;  
  
endmodule
```



Equality

- Logical equality (== and !=)
 - Used in expressions to compare two values
 - Return 0 or 1 when there is no any x or z bit in the operands
 - Return a value of x when an x or z in either operand
 - Net or register operands are treated as unsigned values
 - Integer operands are signed values
- Case equality (=== and !==) — **Not synthesizable, simulation only**
 - Compare both operands bit-by-bit, including x and z
 - $x === x$ and $z === z$
 - Return 1 if all bits are identical; return 0 if there exists an difference

Reduction

- Unary operators

- Operating on a single vector and producing a single-bit result
- If any bit in the operand is x or z, the result is x

- Reduction AND (&)

- If any bit in the operand is 0, the result is 0; otherwise 1
 - e.g., &4'b1010 => 0; &4'b1111 => 1

- Reduction NAND (~&)

- Invert of reduction AND

- Reduction OR (|)

- If any bit in the operand is 1, the result is 1; otherwise 0
 - e.g., |4'b1010 => 1; |4'b0000 => 0

- Reduction NOR (~|)

- Invert of reduction OR

- Reduction XOR (^)


- If there is even number of 1 bits in the operand, the result is 0; otherwise 1
 - e.g., ^4'b1010 => 0; ^4'b1110 => 1

- Reduction XNOR (~^ or ^~)

- Invert of reduction XOR

Example

```
module reduction (a, and_rslt, nand_rslt, or_rslt, nor_rslt, xor_rslt, xnor_rslt);  
  input [3:0] a;  
  output and_rslt, nand_rslt, or_rslt, nor_rslt, xor_rslt, xnor_rslt;  
  assign and_rslt = &a; //reduction AND  
  assign nand_rslt = ~&a; //reduction NAND  
  assign or_rslt = |a; //reduction OR  
  assign nor_rslt = ~|a; //reduction NOR  
  assign xor_rslt = ^a; //reduction exclusive-OR  
  assign xnor_rslt = ^~a; //reduction exclusive-NOR  
endmodule
```

 

Shift



<Left operand> << <shift amount>

<Left operand> >> <shift amount>

- Logical shift operators
 - Bits in the <left operand> are shifted to left or right with 0s fillings
 - High-significant or low-significant bits are lost
- <Shift amount>: the number of positions shifted
 - Can be an expression
 - Always treated as unsigned numbers
 - If there exists any **x** or **z** bit, the result will be unknown

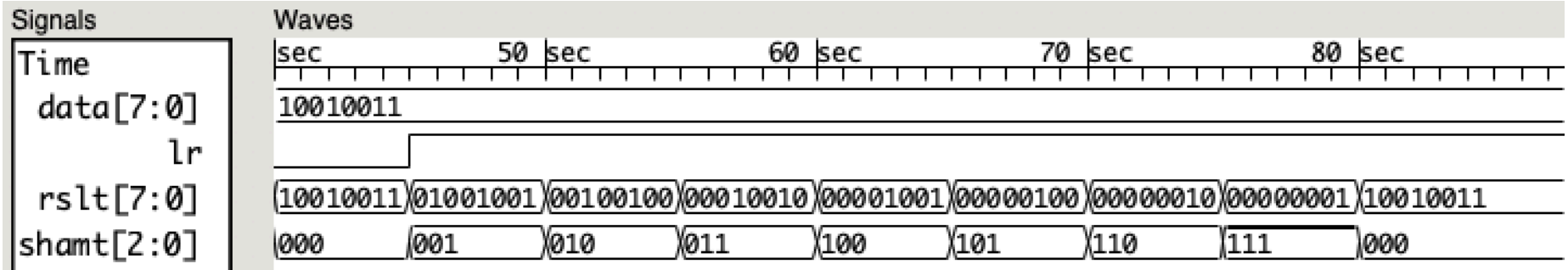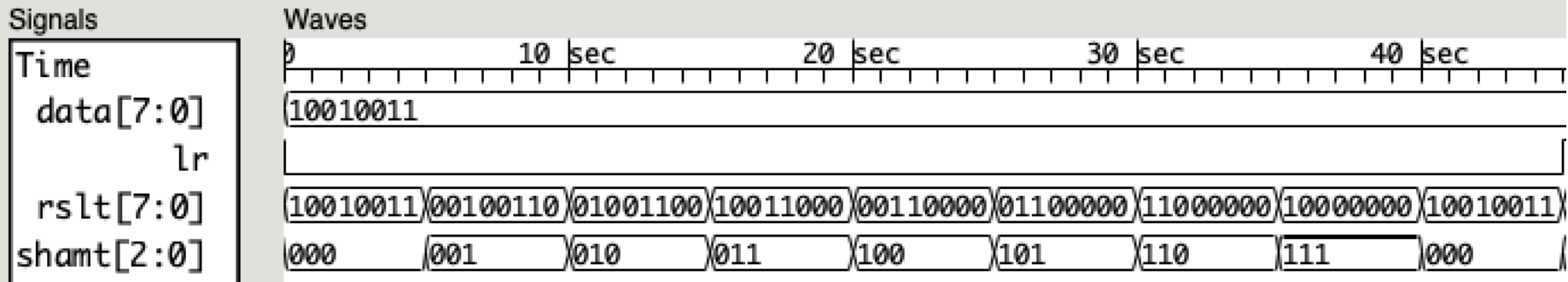Example

```
module shift(data, shamt, rslt, lr);  
  input [7:0] data;//left operand  
  input [2:0] shamt;//shift amount  
  output [7:0] rslt;  
  input      lr; //0: shift left; 1: shift right  
  assign rslt = (lr == 1'b0)? (data << shamt):(data >> shamt);  
endmodule
```



Conditional

- Syntax:

`<conditional expression>?<true expression>:<false expression>`

- Conditional operators can be nested
- Operation:
 - `<conditional expression>` is evaluated to choose the result of `<true expression>` or of `<false expression>`
 - If `<conditional expression>` is evaluated to `x`, the results of both `<true expression>` and `<false expression>` will be applied to a **special bitwise** operator
 - $1 \diamond 1 = 1$
 - $0 \diamond 0 = 0$
 - Otherwise $\Rightarrow x$

Example

```

module mux4bit(in0, in1, sel, out);
  input [3:0] in0, in1;
  input      sel;
  output [3:0] out;
  assign out = sel?in0:in1;
endmodule


```

```

mux4bit M(.in0(in0[3:0]), .in1(in1[3:0]),
          .sel(sel[0]), .out(out));
initial begin
  for (in0 = 0; in0 < 16; in0 = in0 + 1)
    for (in1 = 0; in1 < 16; in1 = in1 + 1)
      for (sel = 0; sel < 2; sel = sel + 1)
        #5;

    #5 $finish;
end

```

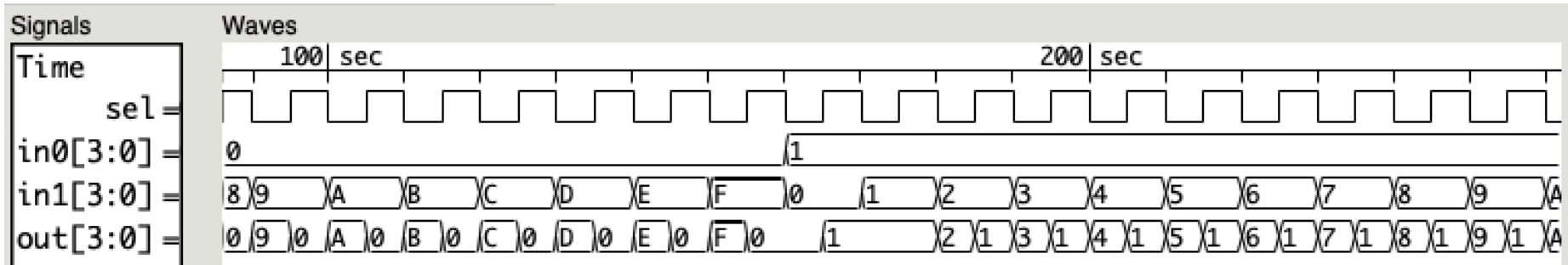

Concatenation

- Form a result from multiple operands
- Syntax:

$\{\text{operand 1, operand 2,}\}$

- The **sizes of operands must be known** before making concatenation
 - E.g., $\{3'b000, 4'hA\} \Rightarrow 7'b0001010$
 - E.g., $\{3'b000, 10\} \Rightarrow \text{error}$
- The size of the result is sum of all sizes of the operands
- Operands are appended from left to right

Replication

- Replicate the pattern a number of times
- Syntax:

$\{\text{rep_number}\{\text{expr1}, \text{expr2}, \dots, \text{exprN}\}\}$

- Similar to the concatenation operator with all operands are the same
 - The sizes of expressions must be known
- Ex:
 - $\{3\{2'b01, 2'b00\}\} \Rightarrow 12'b0100_0100_0100$
 - $\{4\{1\}\} \Rightarrow \text{error}$

Design examples

- **Example 1:** design and implement an 4-bit full adder
- **Answer:**



```
module adder4b (Sum, Cout, A, B, Cin);  
  input  [3:0] A, B;  
  input  Cin;  
  output [3:0] Sum;  
  output Cout;  
  assign {Cout, Sum} = A + B + Cin;  
endmodule
```

Design examples

- **Example 2:** Design a multiply-accumulate (MAC) unit that computes

$$Z[7 : 0] = A[3 : 0] \times B[3 : 0] + C[7 : 0]$$

It sets overflow to one, if the result cannot be represented using 8 bits.


- **Answer:**




```
module mac(output [7:0] Z, output Ovflw,  
           input [3:0] A, B, input [7:0] C);  
    wire [8:0] P;  
    assign P = A*B + C;  
    assign Z = P[7:0];  
    assign Ovflw = P[8];  
endmodule
```

Latch

 - Output Q is keep unchanged when Enable is not active; otherwise input D is transfer to Q


 
```
module latch(output Q, input D, Enable);  
    assign Q = Enable ? D : Q;  
endmodule
```



Exercise: Rock - Paper - Scissors

- In Vietnamese: oẳn - tù - à

`module rps(win, player, p0guess, p1guess);`

- Assumptions:
 - Input: `p0guess, p1guess` = {0 for rock, 1 for paper, 2 for scissors}
 - Output: `player` is 0 if p0 wins, 1 if p1 wins, and don't care if there is a tie
 - Output: `win` is 0 if there is a tie and 1 if a player wins
- Reminders
 - Paper beats rock, scissors beats paper, rock beats scissors
 - Same values tie

Summary

- RTL model
 - Use continuous assignment: assign
 - Combinational circuits only
 - Operators
 - Operands

The end

