

DIGITAL DESIGN WITH HDL


Chapter 1: Fundamentals




Design methodologies

- Two design methodologies:
 - Top-down design
 - Top-level block is identified
 - Next lower-level are defined
 - Bottom-level contains blocks cannot be further divided
 - Bottom-up design
 - The lowest level - leaf cells - is defined first
 - These blocks are used to build the next higher levels
 - Continue until the top-level block reached

Top-down design

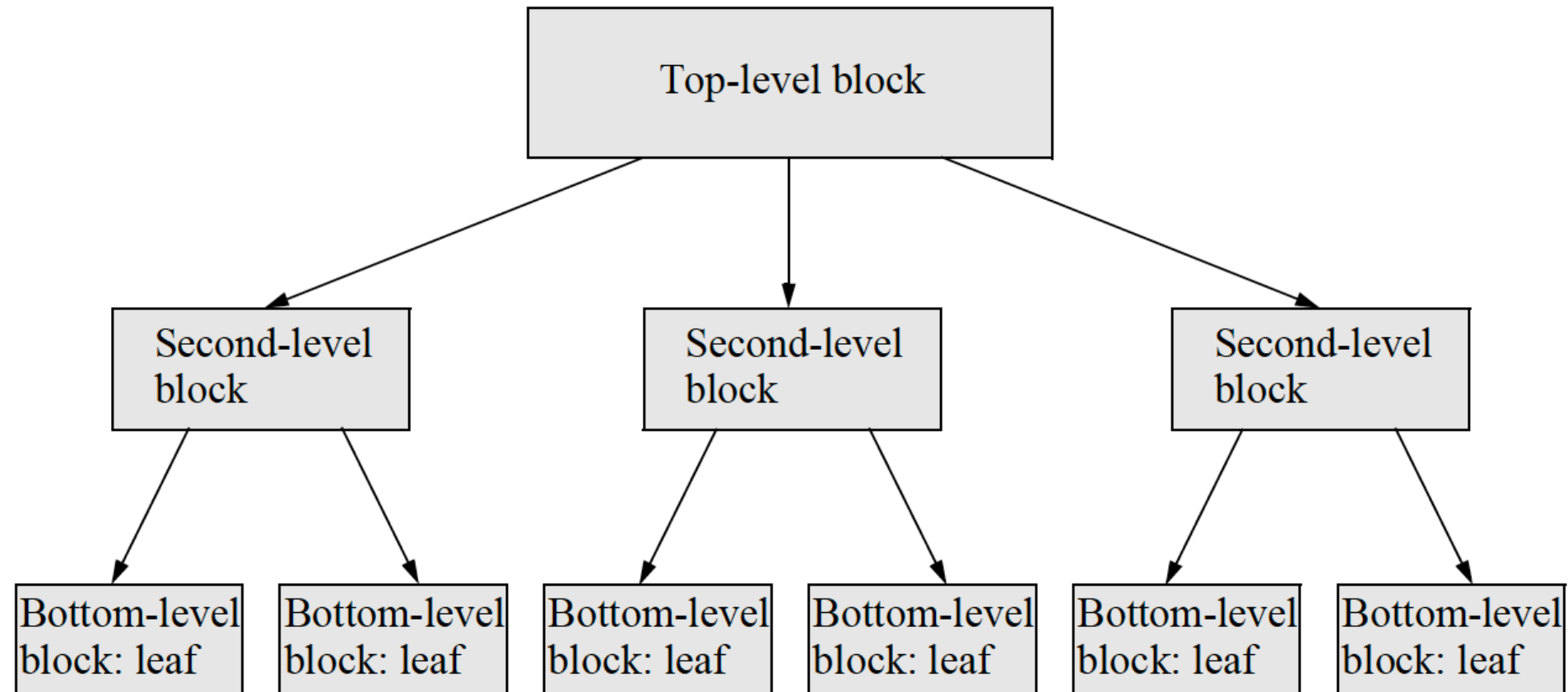


Bottom-up design

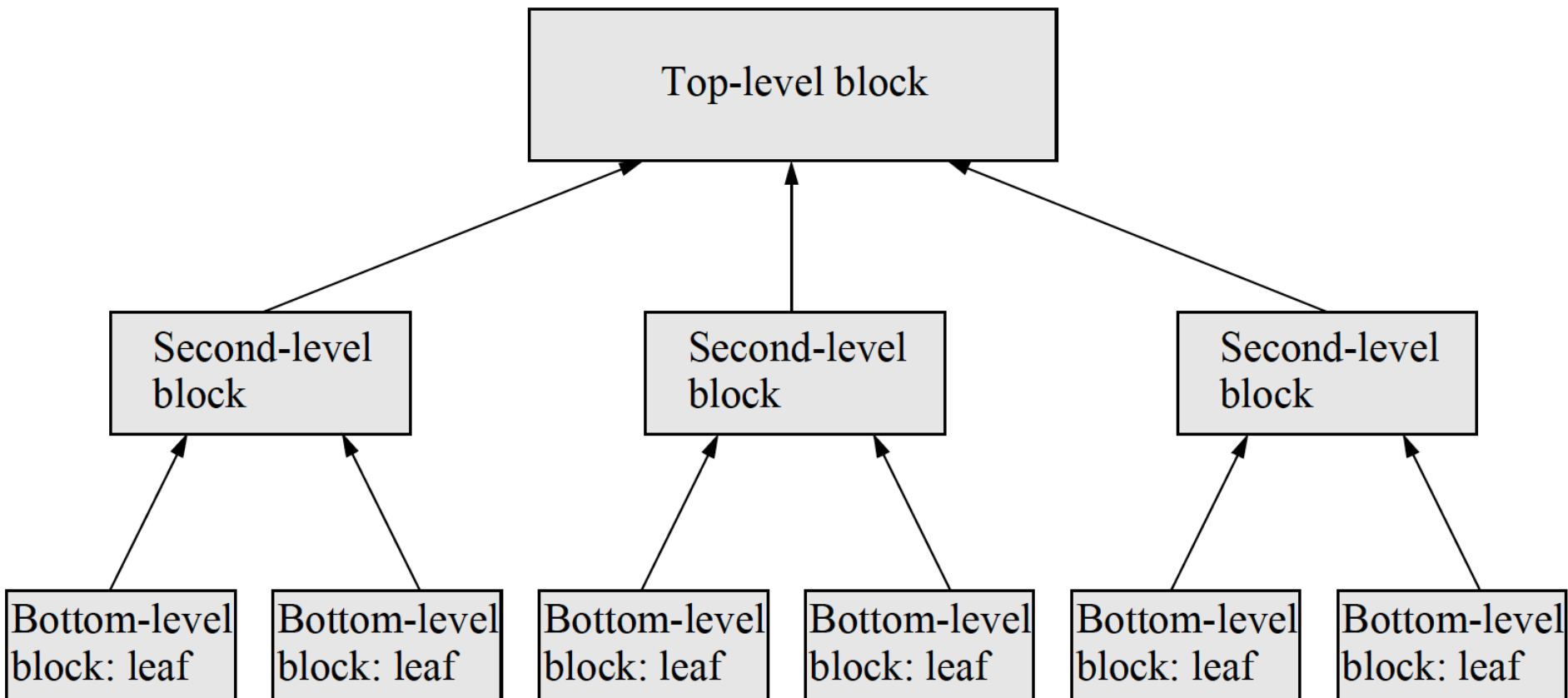

Overview of HDLs

- Hardware description languages (HDLs)
 - Are computer-based hardware description languages
 - Allow modeling and simulating the functional behavior and timing of digital hardware
 - Synthesis tools take an HDL description and generate a technology-specific netlist
- Two main HDLs used by industry
 - Verilog HDL (C-based, industry-driven)
 - VHSIC HDL or VHDL (Ada-based, defense/industry/university-driven)

Why HDLs?

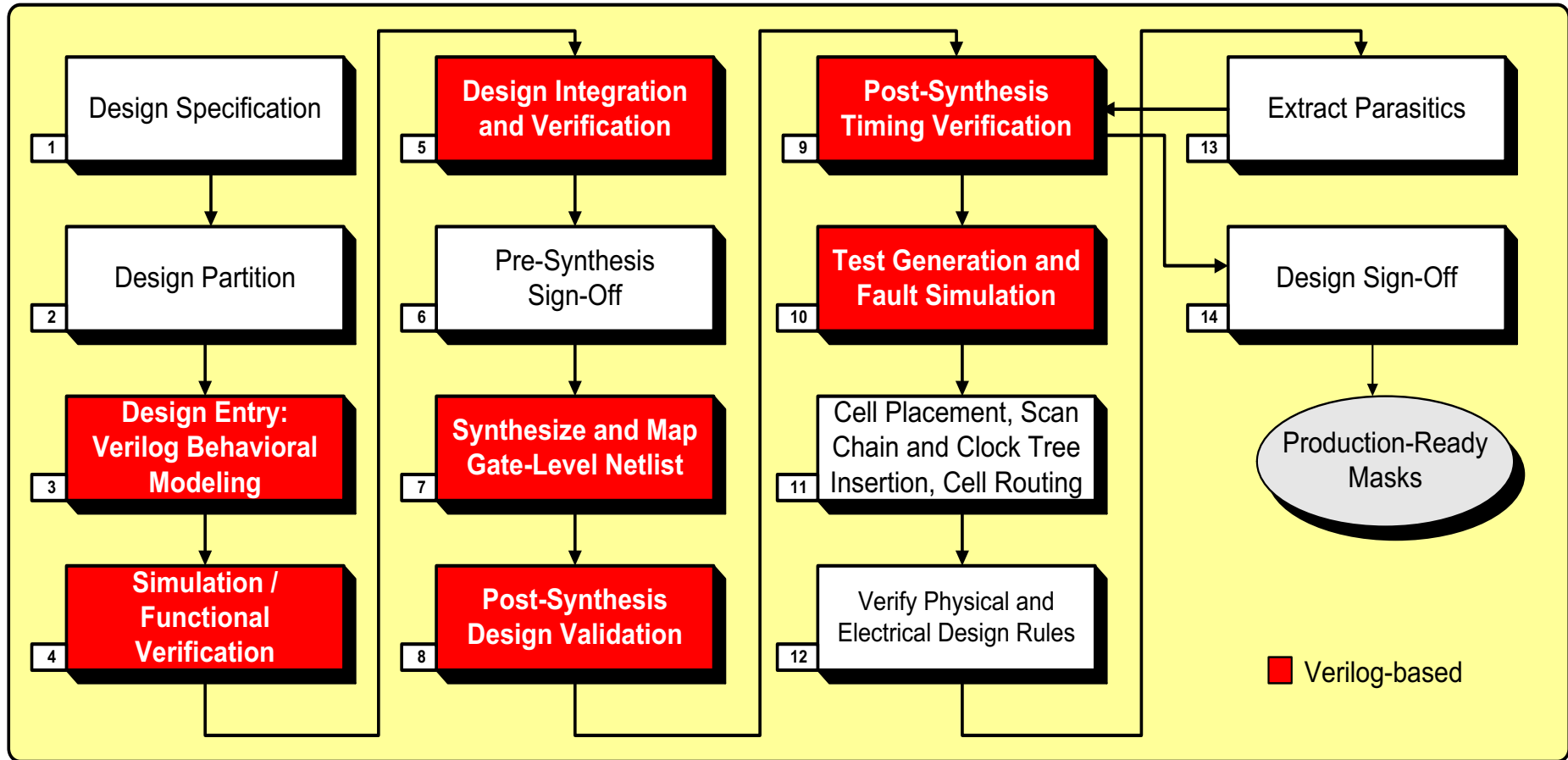


Why HDLs

- Takes a description of what a circuit does
- Creates the hardware to do it (semi-) automatically
 - During the synthesis process

```
if (a) f = c & d;  
else if (b) f = d;  
else f = d & e;
```

Synthesis process

 

Verilog


- In this class, we will use the Verilog HDL
 - Used in academia and industry
 - Many principles we will discuss apply to any HDL
 - Once you can “think hardware”, you should be able to use any HDL fairly quickly
- Provides many descriptive styles
 - Structural
 - Register Transfer Level (RTL)
 - Behavioral
- C-like language
 - **NOT** programming language



Verilog module

- A circuit is a **module**
 - Could be simple or complex


 
```
module decoder_2_to_4 (A, D);  
  
input [1:0] A ;  
output [3:0] D ;  
  
assign D = (A == 2'b00) ? 4'b0001:  
           (A == 2'b01) ? 4'b0010:  
           (A == 2'b10) ? 4'b0100:  
           (A == 2'b11) ? 4'b1000;  
  
endmodule
```



Module template

```
module <module name> (port list);  
    declarations  
        reg, wire, parameter,  
        input, output, . . .  
        . . .  
    <module internals>  
        statements  
        initial, always, module instantiation, . . .  
        . . .  
endmodule
```

Verilog module example

 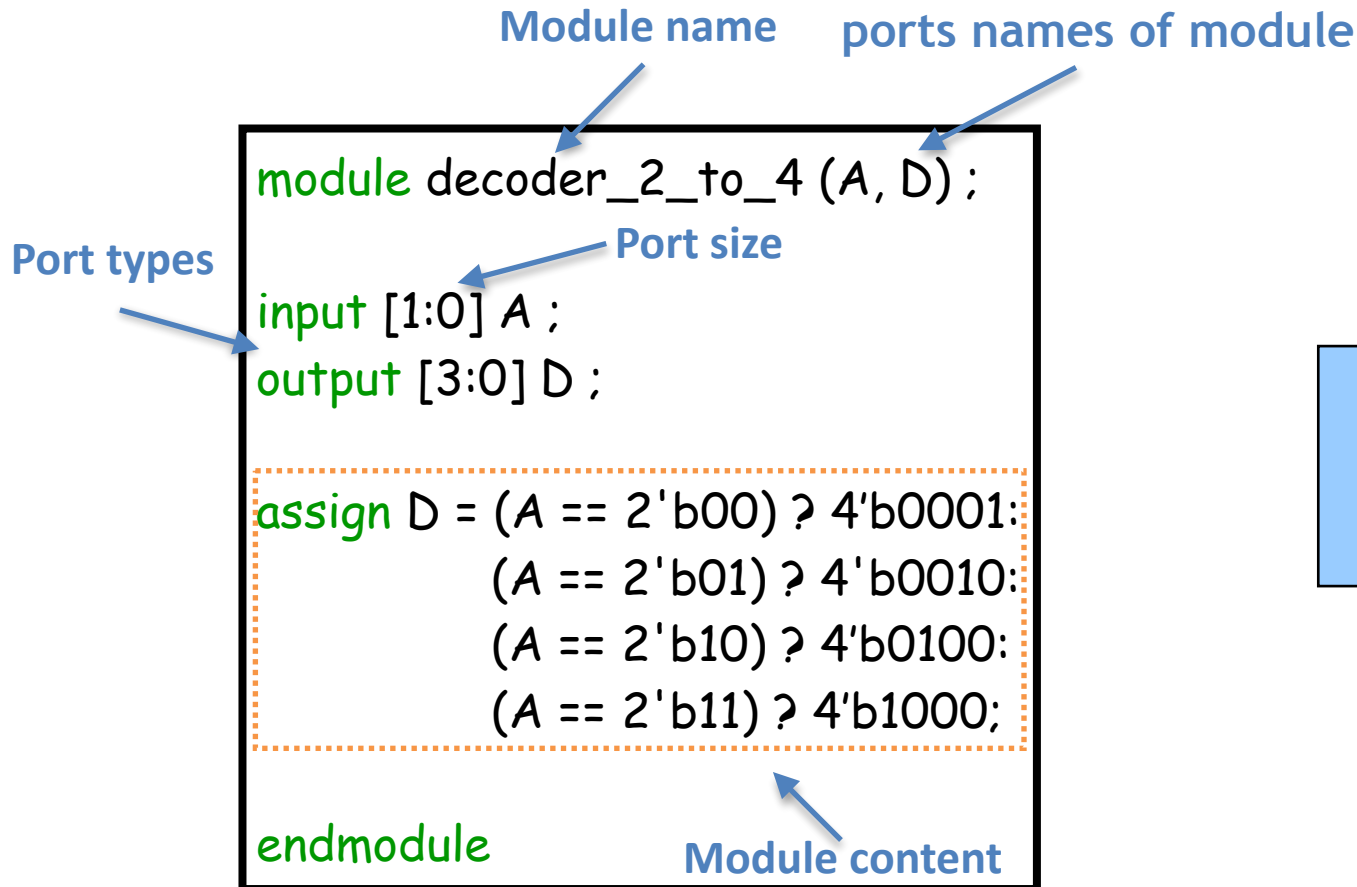

Declaring a module

1. Start with the **module** keyword
2. Choose a **descriptive** module name (different from **keywords**)
3. Declare the ports (connectivity)
 - Choose **descriptive** signal names
 - Define types and size
4. Declare any internal signals
5. Write the content/functionality (the course)
6. Finalize by the **endmodule** keyword

Ports

- A signal is attached to every port
- Port types:
 - **input**: receiving arrival information
 - **output**: providing results
 - **inout**: functioning as both input or output (rarely used)
- Port size
 - Scalar: single bit (by default)
 - **input** cin;
 - Vector: multiple bits (bus), must specify
 - Syntax: [MSB:LSB]
 - Size: $| \text{MSB} - \text{LSB} | + 1$
 - Example:
 - **output** [3:0] sum;
 - **input** [1:4] a, b;

Module styles

- Modules (content/functionality) can be specified different ways
 - **Structural** – connect primitives and modules
 - **RTL** (Register transfer level) – use continuous assignments
 - **Behavioral** – use initial and always blocks
- A single module can use more than one method!

Structure model

- A schematic in text form
- Structural module can be designed using (**instances**):
 - **Primitive** gates (predefined simple gates)
 - User defined modules (previously designed and tested)
- Interconnections between instances are specified using **nets** data-type

Structural model example

```
module majority (major, V1, V2, V3);
```

```
    output major;
```

```
    input V1, V2, V3;
```


```
    wire N1, N2, N3;
```

```
    and A0 (N1, V1, V2),  
         A1 (N2, V2, V3),  
         A2 (N3, V3, V1);
```

```
    or Or0 (major, N1, N2, N3);
```

```
endmodule
```

instances

 

RTL model

- Data flow model
 - Design combinational logic only
 - Higher level of abstraction than the structural model
- Using the continuous assignment statement **assign**
 - Operators are used to make expressions

RTL model example


```
module majority (major, V1, V2, V3) ;
```

```
output major ;
```

```
input V1, V2, V3 ;
```

```
assign major = V1 & V2  
              | V2 & V3  
              | V1 & V3;
```

```
endmodule
```

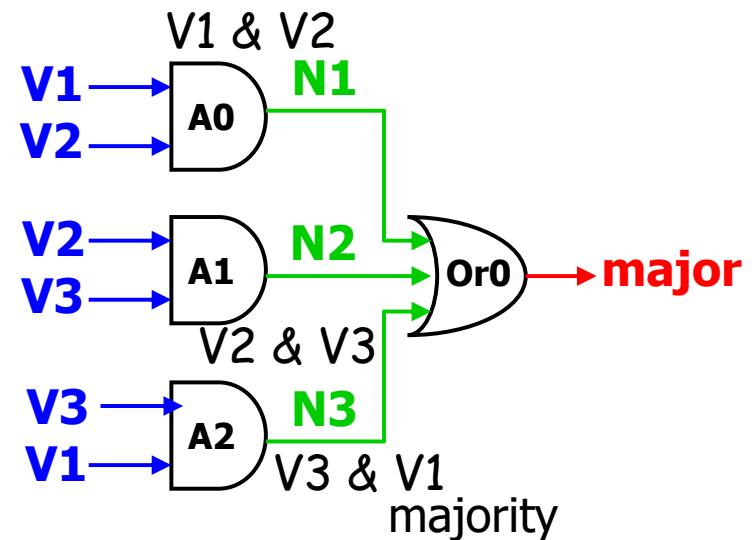

Behavioral model

- Behavioral modeling is an abstraction of the functional operation of the design
 - Do not describe the implementation of the design
 - Outputs are characterized by their relationship to the inputs
 - Use **initial** and **always** statements
 - Procedural constructs

Behavioral model example

```
module majority (major, V1, V2, V3) ;
```

```
output reg major ;
```

← New output type “reg” used to store values

```
input V1, V2, V3 ;
```

```
always @(V1, V2, V3) begin
```


```
    if (V1 && V2 || V2 && V3  
        || V1 && V3) major = 1;  
    else major = 0;
```

```
end
```

```
endmodule
```

Relationship between the output and
their inputs

One more example

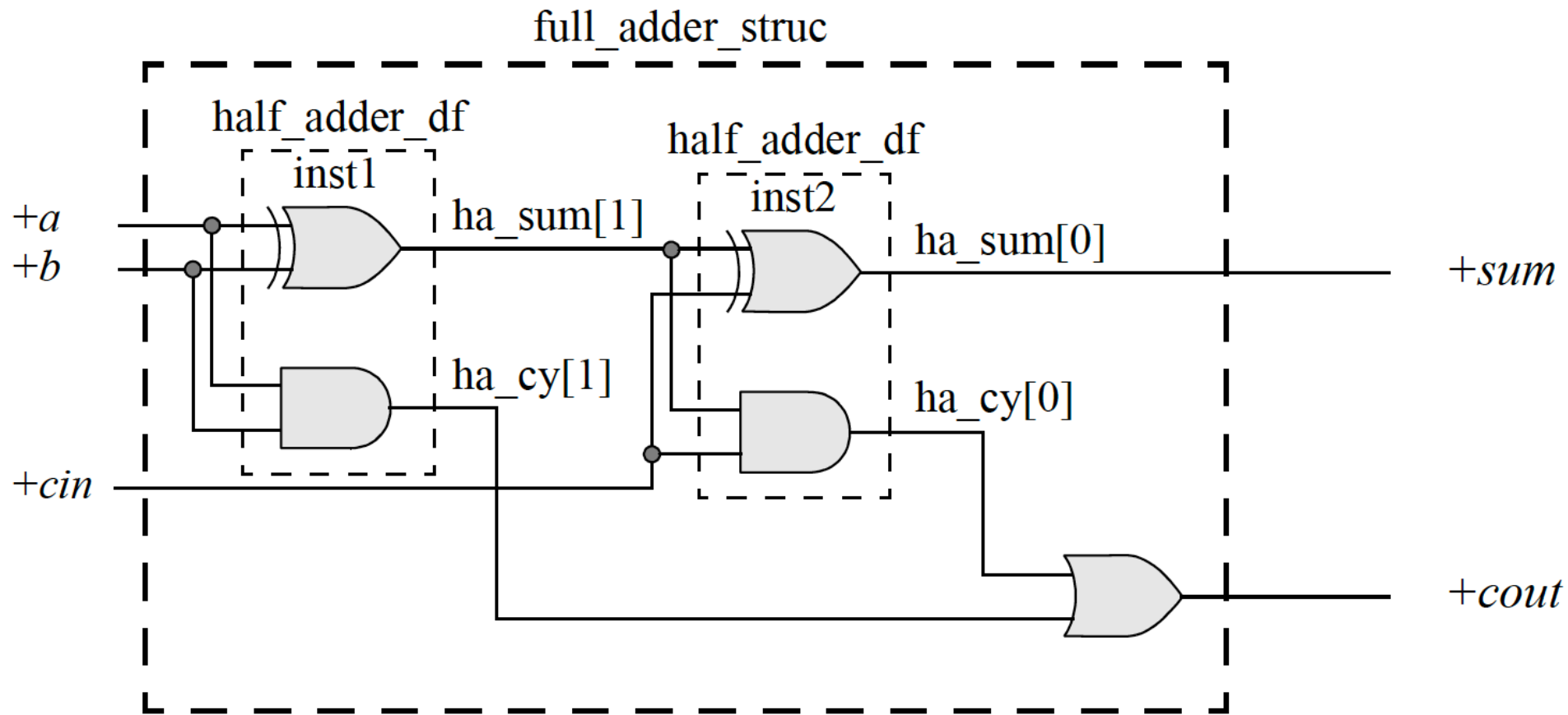

The full adder circuit

Structural model implementation

```
module fulladder_struc(a, b, cin, sum, cout);  
    input a, b, cin;  
    output sum, cout;  
    wire ha_sum_1, ha_cy_1, ha_cy_0;
```

```
    xor(ha_sum_1, a, b);  
    and(ha_cy_1, a, b);
```

half_adder_df sub-module

```
    xor(sum, ha_sum_1, cin);  
    and(ha_cy_0, ha_sum_1, cin);
```

half_adder_df sub-module

```
    or(cout, ha_cy_1, ha_cy_0);
```

```
endmodule
```


RTL model implementation

```
module fulladder_rtl(a, b, cin, sum, cout);  
    input a, b, cin;  
    output sum, cout;  
  
    assign sum = a ^ b ^ cin;  
    assign cout = (a & b) | (a & cin) | (b & cin);  
  
endmodule
```

$$\text{cout} = (a \oplus b) \cdot \text{cin} + a \cdot b = (a \cdot b) | (a \cdot \text{cin}) | (b \cdot \text{cin})$$

Behavioral model implementation

```
module fulladder_bhv(a, b, cin, sum, cout);  
    input a, b, cin;  
    output reg sum, cout;  
  
    always @(a, b, cin) begin  
        sum = a ^ b ^ cin;  
        cout = (a & b) | (a & cin) | (b & cin);  
    end  
  
endmodule
```

Hierarchy design

```
module half_adder_struc(a, b, sum, cout);
```


```
  input a, b;
```

```
  output sum, cout;
```

```
  xor(sum, a, b);
```

```
  and(cout, a, b);
```

```
endmodule
```

 

```
module fulladder_struc(a, b, cin, sum, cout);
```

```
  input a, b, cin;
```

```
  output sum, cout;
```

```
  wire c1, c2, s2;
```

Instance name

```
  half_add_struc PARTSUM(a, b, s1, c1);
```



```
  half_add_struc SUM(s1, cin, sum, c2);
```

```
  or(cout, c2, c1);
```

```
endmodule
```

Verification by simulation

 
 
- Testing a designed module to ensure its operations
 - Applying stimulus to inputs and checking outputs
- Use a test bench module
 - An instantiation of a unit under test
 - Verilog code to generate stimulus
 - Verilog code to monitor and display the response
 - Text
 - Waveform



```
#0 x1=1'b0; x2=1'b0; x3=1'b0;  
#10 x1=1'b0; x2=1'b0; x3=1'b1;  
#10 x1=1'b0; x2=1'b1; x3=1'b0;
```

Hierarchical & source code

  - Can have **all modules in a single file**
 - Module order doesn't matter!
 - Good for small designs
 - Not so good for bigger ones
 - Not so good for module reuse (cut & paste)
- Can **break up modules into multiple files**
 - Helps with organization
 - Lets you find a specific module easily
 - Great for module reuse (add file to project)



The end

