

DIGITAL DESIGN WITH HDL

Chapter 2: Structural model design



Structure model

- A schematic in text form
- Structural module can be designed using (**instances**):
 - **Primitive** gates (predefined simple gates)
 - User defined modules (previously designed and tested)
- Interconnections between instances are specified using **nets** data-type

Structural model - design steps

1. Create module interface
 - Define the module name
 - Declare the port list
2. Declare the internal **wires** needed to connect gates
3. Instantiate the **primitive gates** in the circuit
4. Instantiate **user defined modules** in the circuit (if required)
5. Put the names of the wires in the correct port locations of the gates
 - For primitives, outputs always come first
 - For user defined instantiation, use connection methods (discussed later)

Example

```
module half_adder_struct(a, b, sum, cout);  
  input a, b;  
  output sum, cout;
```

```
  xor(sum, a, b);  
  and(cout, a, b);
```

```
endmodule
```

Connection wires →

User defined modules →

Primitive gates →

```
module fulladder_struct(a, b, cin, sum, cout);  
  input a, b, cin;  
  output sum, cout;  
  wire c1, c2, s1;
```

```
  half_add_struct PARTSUM(a, b, s1, c1);  
  half_add_struct SUM(s1, cin, sum, c2);
```

```
  or(cout, c2, c1);
```


```
endmodule
```

Primitive gates

- Verilog provides a set of gate primitives (part of language)
 - One or more scalar inputs and only one scalar output
 - eg. **and**, **nand**, **or**, **nor**, **xor**, **xnor**, **not**, **buf**, etc.
 - Names of primitive are **keywords**
 - Known “behavior”
 - Cannot access “inside” description
- Can also model at the transistor level
 - Most people don’t, we won’t
- Note: Flip-flops are not primitives

Primitive gates

 - Output port is always the first port
 - Inputs follows (unlimited) - except **not**
- Optional: instantiation name & delay



nand (y, a, b, c);

nand N1 (y, a, b, c);

Optional instantiation name Inputs


syntax:

```
gate_type delay inst1 (output_1, input_11, input_12, ..., input_1n),
                    delay inst2 (output_2, input_21, input_22, ..., input_2n),
                    ...
                    delay instm (output_m, input_m1, input_m2, ..., input_mn);
```

Optional

Gate delay

 - All gates have propagation delay
 - Time for processing signals
 - Technology-dependent
 - Only simulation cares delay
 - Synthesis process will not take into account
- Types of delay
 - Rise delay: $0 \rightarrow 1$
 - Fall delay: $1 \rightarrow 0$
 - Turn-off delay: $0,1 \rightarrow x,z$



Gate delay - Verilog


- Can specify all three types of delay
 - But, mainly use one value for all

Syntax: #(rise, fall, turn-off)

Mainly used: #delay

- Notes:
 - All values must be constant expression
 - Can be specify more precisely: <minimum : typical : maximum>


Example

 

```

module log_eqn_sop8 (x1, x2, x3, x4, z1);
  input x1, x2, x3, x4;
  output z1;
  wire net1, net2;
  and #3 inst1 (net1, x1, x2);
  and #3 inst2 (net2, ~x3, x4);
  or #5 inst3 (z1, net1, net2);
endmodule

```

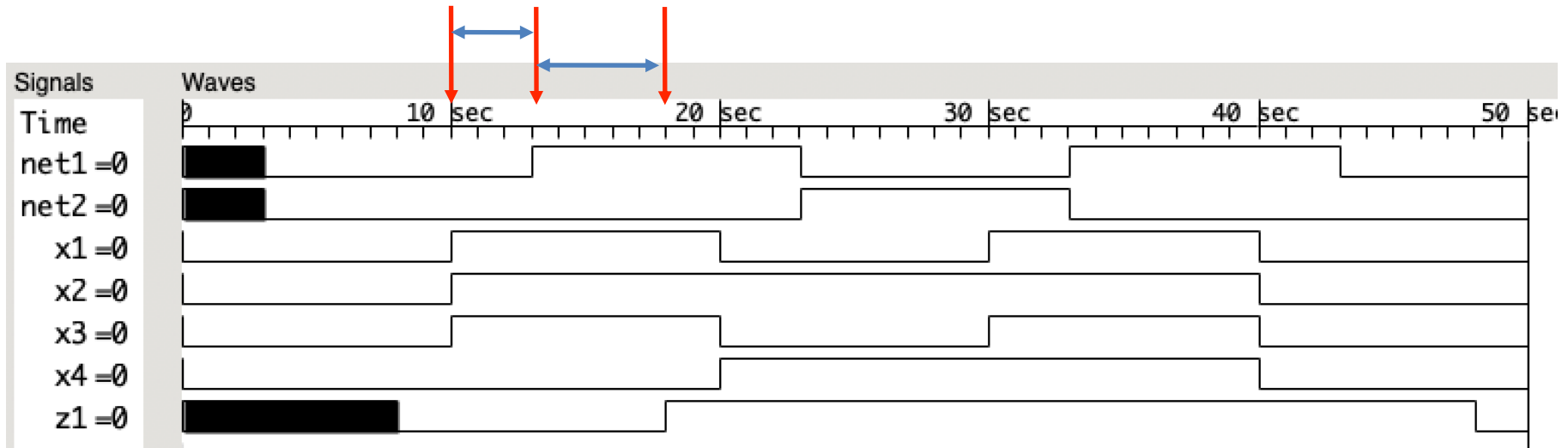

Waveform generated by icarus-verilog and displayed by gtkwave

Data types: *wire*

- Verilog defines two data types
 - Net: physical wire or group wires (bus) for connecting hardware elements
 - *wire, tri, wand,...*
 - Register: storage elements whose values are retained until updated
 - *reg*
- Structural model uses only net data type, especially *wire*
 - Values are determined by logic driving the net

Scalar & vector signals



- Scalar: signal bit - do not need to specify the size
 - `wire a;` //the size of signal a is one bit
- Vector: multiple bit (bus) - specify size using range
 - Syntax: $[MSB: LSB]$
 - $MSB, LSB \in \mathbb{Z}$, constant expression
 - Size of the vector: $|MSB - LSB| + 1$
 - $MSB > LSB$ ✓
 - $MSB < LSB$ ✓
 - Example:
 - `wire [3:0] a;` //4 bit a bus
 - `wire [1:4] b;` //4 bit b bus
 - Can access the whole vector, a part of vector, or a single bit

Vectors

- Part select
 - Syntax: `<name>[MSB: LSB]`
 - The relationship between MSB and LSB must be in accordance with declaration
 - Example:
 - `wire [3:0] a;`
 - `a[3:1];` //correct part-select
 - `a[1:2];` //wrong part-select because of reverse order
 - `a[4:2];` //wrong part-select because of out-of-range
- Bit select
 - Syntax: `<name>[position]`
 - Example: `a[1]; a[3];`

Connections

  - Port connection rules
 - **input:**
 - Internally: net
 - Externally: reg or net
 - **output:**
 - Internally: reg or net
 - Externally: net
 - **inout:**
 - Internally/externally: net
- Error messages will be indicated if violated




Intermodules connections

- **Method 1:** positional or implicit connections
 - Used for the primitive gates (no choice)
 - Look like function/procedure call in software
 - Acceptable with few ports or interchangeable ports
 - Need to remember the position of each port
- **Method 2:** connecting by port names
 - Easy to read and manage
 - No need to follow the order of ports declared
 - Syntax: `.<port name>(<connected signal>)`

 Example

```
module decoder(In, En, Out);  
    input [1:0] In;  
    input En;  
    output [3:0] Out;  
    ....  
endmodule
```

```
module positional(...);  
    wire [1:0] pIn;  
    wire pEn;  
    wire [3:0] pOut;  
    ....  
    decoder D1(pIn, pEn, pOut);  
endmodule
```



```
module name(...);  
    wire [1:0] nIn;  
    wire nEn;  
    wire [3:0] nOut;  
    ....  
    decoder D1(.En(nEn),  
                .In(nIn),  
                .Out(nOut));  
endmodule
```

Empty port connections

- General rules of unconnected ports
 - Input: high-impedance state (high-Z)
 - Output: unused port
- Note: do not leave an input port empty due to unmanageable high-Z states
 - Connect the input to the inactive value
 - Active high $\Rightarrow 0$; active low $\Rightarrow 1$
- Make a port unconnected
 - Position method: a blank between two commas
 - `decoder D1(pIn, , pOut);`
 - Name method: empty signal name
 - `decoder D1(.In(nIn), .En(), .Out(nOut));`

Hierarchy and scope


- A module cannot access “internal” signals of instantiations
 - Must make a port when needed

```
module add8bit(cout, sum, a, b);  
    output [7:0] sum;  
    output cout;  
    input [7:0] a, b;  
    wire cout0, cout1,... cout6;  
    FA A0(cout0, sum[0], a[0], b[0], 1'b0);  
    FA A1(cout1, sum[1], a[1], b[1], cout0);  
    ...  
    FA A7(cout, sum[7], a[7], b[7], cout6);  
endmodule
```

To access **cout6** when
instantiating the **add8bit** must
output **cout6**

Design example

- A 4:1 multiplexer diagram

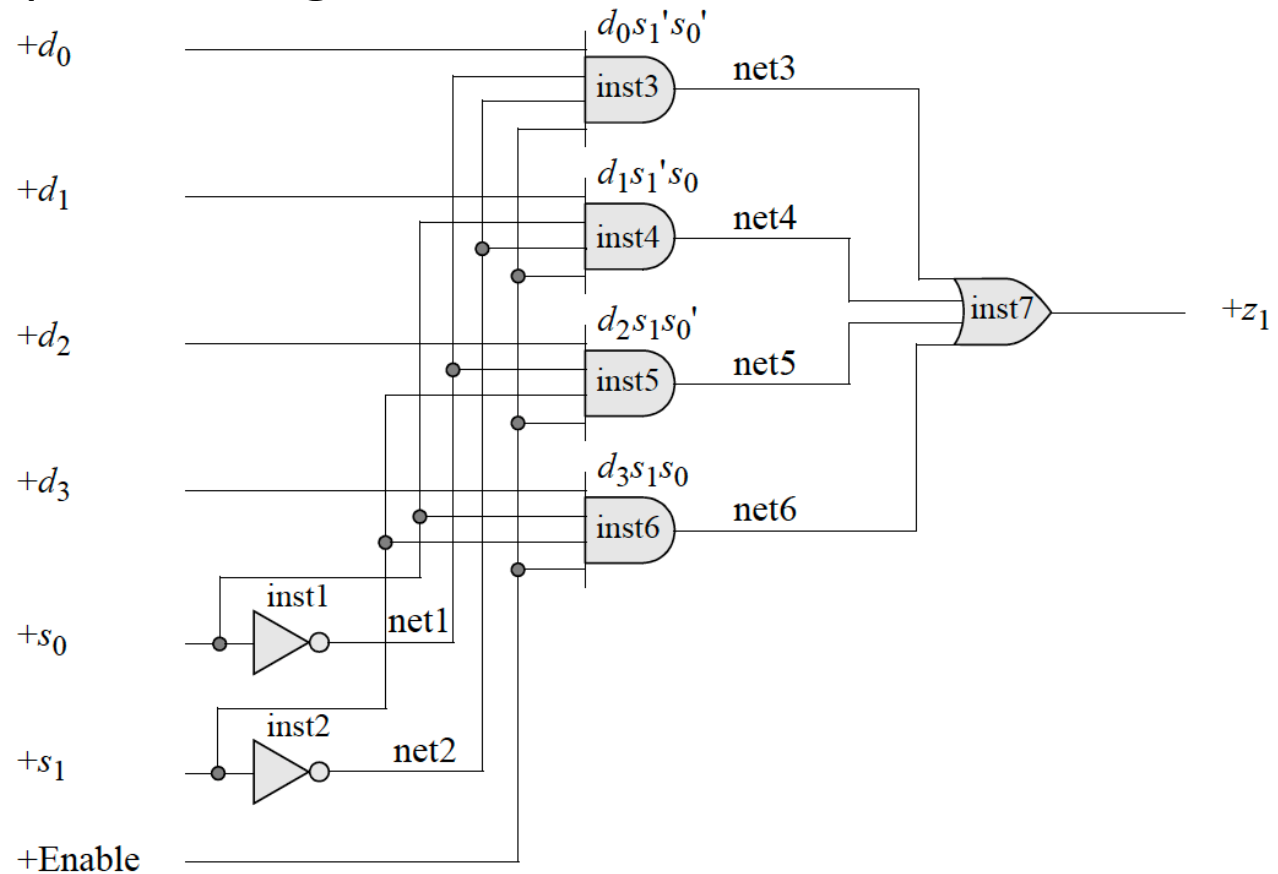

Design example - Verilog code

```
module mux_4to1 (d, s, enbl, z1);  
    input [3:0] d;  
    input [1:0] s;  
    input enbl;  
    output z1;  
  
    not inst1 (net1, s[0]),  
        inst2 (net2, s[1]);  
  
    and inst3 (net3, d[0], net1, net2, enbl),  
        inst4 (net4, d[1], s[0], net2, enbl),  
        inst5 (net5, d[2], net1, s[1], enbl),  
        inst6 (net6, d[3], s[0], s[1], enbl);  
  
    or inst7 (z1, net3, net4, net5, net6);  
endmodule
```

Exercise 1

- Using Verilog HDL to implement a three bit comparator that consists of two 3-bit inputs a, b and three 1-bit output a_lt_b, a_eq_b, and a_gt_b to indicate if a is less than b, a is equal to b, and a is greater than b, respectively. Given that the following boolean expressions can be used to compare (a[2], b[2] : MSB):


$$(a < b) = \overline{a[2]} \cdot b[2] + \overline{a[2]} \oplus \overline{b[2]} \cdot \overline{a[1]} \cdot b[1] \\ + \overline{a[2]} \oplus \overline{b[2]} \cdot \overline{a[1]} \oplus \overline{b[1]} \cdot \overline{a[0]} \cdot b[0]$$

$$(a = b) = \overline{a[2]} \oplus \overline{b[2]} \cdot \overline{a[1]} \oplus \overline{b[1]} \cdot \overline{a[0]} \oplus \overline{b[0]}$$

$$(a > b) = a[2] \cdot \overline{b[2]} + \overline{a[2]} \oplus \overline{b[2]} \cdot a[1] \cdot \overline{b[1]} \\ + \overline{a[2]} \oplus \overline{b[2]} \cdot \overline{a[1]} \oplus \overline{b[1]} \cdot a[0] \cdot \overline{b[0]}$$

Exercise 2

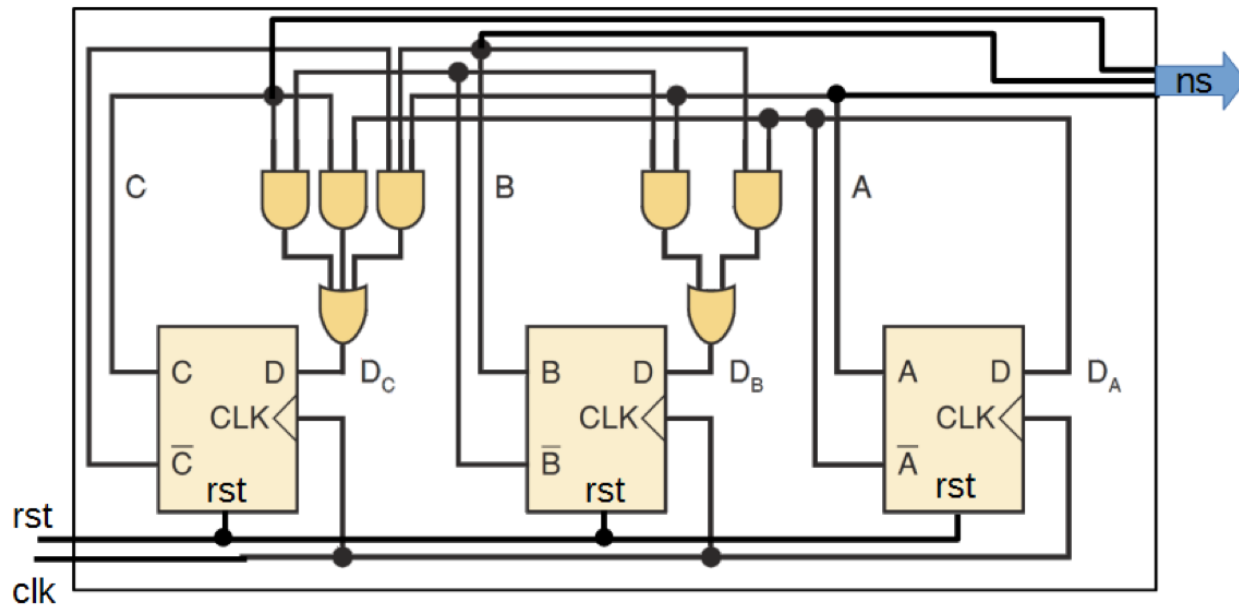2. Using Verilog HDL to implement a mod 8 counter whose diagram is shown as follow. Assume that there exist a D-flip-flop module whose interface is shown below



```
module dff(input clk, d, output q, input rst);
```

The end

